
MUX circuit using schematic, and some different english languages

Logic Design


"It's a MUX"

"It works like a switch"

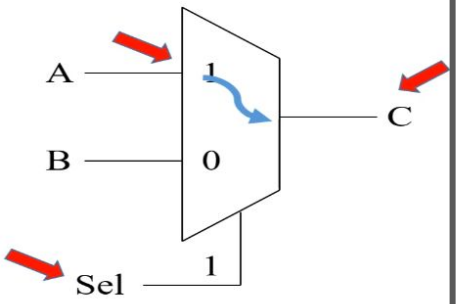"The output C, gets either the input A or B depending on the value of Select"



Logic Gates

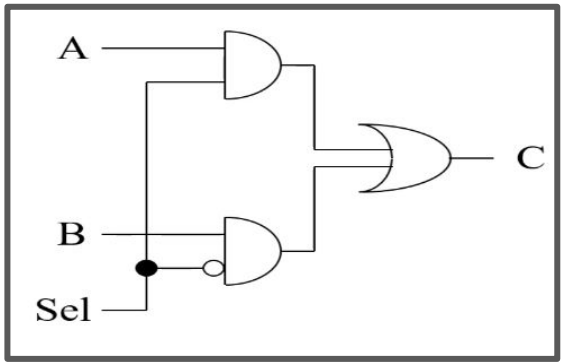

FPGA LUT

A	B	Sel	C
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1